

# CEDT – Digital Logic 2023

## Day 4

### Combinatorial Logic Case Studies

### Arithmetic's

# Combinational logic design case studies

- General design procedure
- Case studies
  - BCD to 7-segment display controller
  - logical function unit
  - process line controller
  - calendar subsystem
- Arithmetic circuits
  - integer representations
  - addition/subtraction
  - arithmetic/logic units


# General design procedure for combinational logic

- 1. Understand the problem
  - what is the circuit supposed to do?
  - write down inputs (data, control) and outputs
  - draw block diagram or other picture
- 2. Formulate the problem using a suitable design representation
  - truth table or waveform diagram are typical
  - may require encoding of symbolic inputs and outputs
- 3. Choose implementation target
  - ROM, PAL, PLA
  - mux, decoder and OR-gate
  - discrete gates
- 4. Follow implementation procedure
  - K-maps for two-level, multi-level
  - design tools and hardware description language (e.g., Verilog)
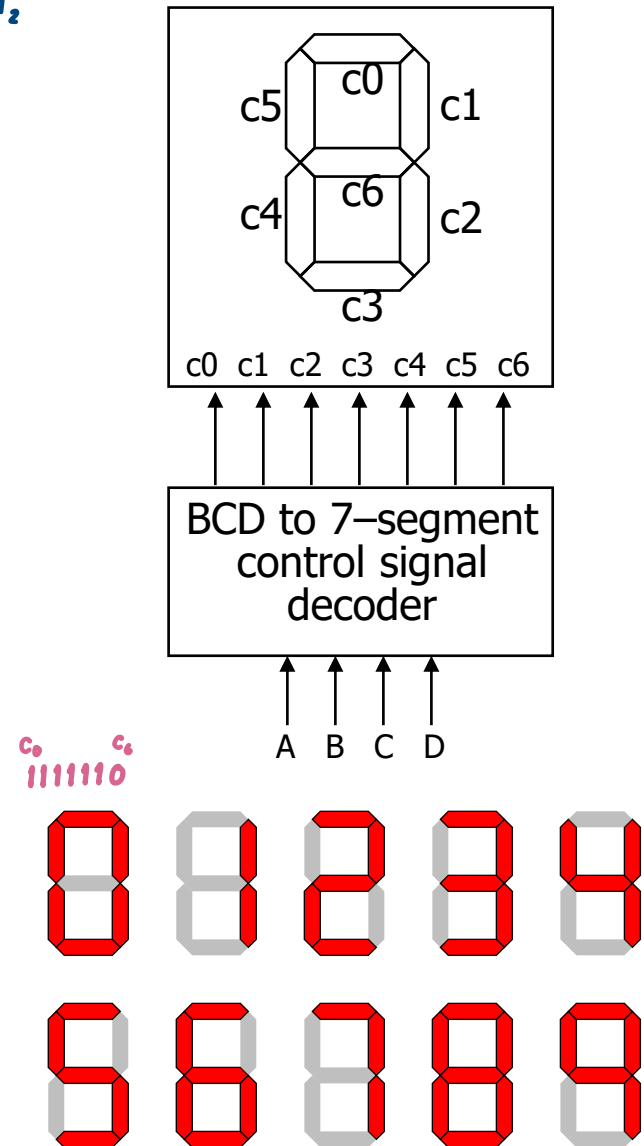
# BCD to 7-segment display controller

BCD  $79_{10} \Rightarrow 0111_2 1001_2$

- Understanding the problem
  - input is a 4 bit bcd digit (A, B, C, D)
  - output is the control signals for the display (7 outputs C0 – C6)
- Block diagram



# Formalize the problem

- Truth table
  - show don't cares
- Choose implementation target
  - if ROM, we are done
  - don't cares imply PAL/PLA may be attractive
- Follow implementation procedure
  - minimization using K-maps

	A	B	C	D	C0	C1	C2	C3	C4	C5	C6
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	0	0	1	1
	1	0	1	—	—	—	—	—	—	—	—
	1	1	—	—	—	—	—	—	—	—	—

# Implementation as minimized sum-of-products

- 15 unique product terms when minimized individually

$C_0$

1	0	X	1
0	1	X	1
1	1	X	X
1	1	X	X

A  
D  
C  
B

$C_1$

1	1	X	1
1	0	X	1
1	1	X	X
1	0	X	X

A  
D  
C  
B

$C_2$

1	1	X	1
1	1	X	1
1	1	X	X
0	1	X	X

A  
D  
C  
B

$C_3$

1	0	X	1
0	1	X	0
1	0	X	X
1	1	X	X

A  
D  
C  
B

$C_4$

1	0	X	1
0	0	X	0
0	0	X	X
1	1	X	X

A  
D  
C  
B

$C_5$

1	1	X	1
0	1	X	1
0	0	X	X
0	1	X	X

A  
D  
C  
B

$C_6$

0	1	X	1
0	1	X	1
1	0	X	X
1	1	X	X

A  
D  
C  
B

$C_0 = A + B D + C + B' D'$   
 $C_1 = C' D' + C D + B'$   
 $C_2 = B + C' + D$   
 $C_3 = B' D' + C D' + B C' D + B' C$   
 $C_4 = B' D' + C D'$   
 $C_5 = A + C' D' + B D' + B C'$   
 $C_6 = A + C D' + B C' + B' C$

# Implementation as minimized S-o-P (cont'd)

## ■ Can do better

- 9 unique product terms (instead of 15)  $\Rightarrow$  Espresso
- share terms among outputs
- each output not necessarily in minimized form

		A			
C2		1	1	X	1
		1	1	X	1
C		1	1	X	X
		0	1	X	X
		B			

		A			
C2		1	1	X	1
		1	1	X	1
C		1	1	X	X
		0	1	X	X
		B			

$$C0 = A + B D + C + B' D'$$

$$C1 = C' D' + C D + B'$$

$$C2 = B + C' + D$$

$$C3 = B' D' + C D' + B C' D + B' C$$

$$C4 = B' D' + C D'$$

$$C5 = A + C' D' + B D' + B C'$$

$$C6 = A + C D' + B C' + B' C$$

$$C0 = B C' D + C D + B' D' + B C D' + A$$

$$C1 = B' D + C' D' + C D + B' D'$$

$$C2 = B' D + B C' D + C' D' + C D + B C D'$$


$$C3 = B C' D + B' D + B' D' + B C D'$$

$$C4 = B' D' + B C D'$$

$$C5 = B C' D + C' D' + A + B C D'$$

$$C6 = B' C + B C' + B C D' + A$$

# PLA implementation

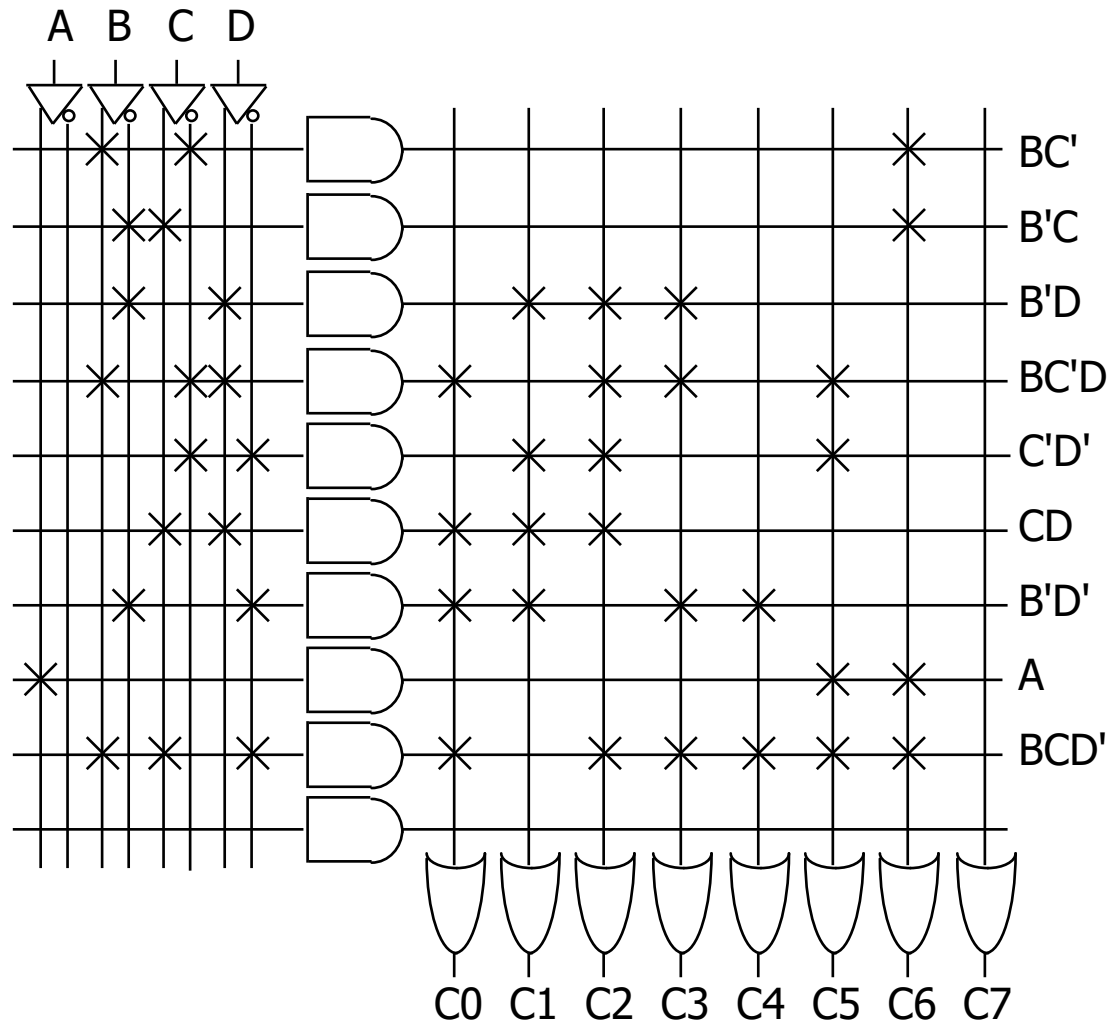



# PAL implementation vs. Discrete gate implementation

- Limit of 4 product terms per output

- decomposition of functions with larger number of terms
- do not share terms in PAL anyway  
(although there are some with some shared terms)

$$C2 = B + C' + D$$

$$C2 = B' D + B C' D + C' D' + C D + B C D'$$

$$C2 = B' D + B C' D + C' D' + W$$

$$W = C D + B C D'$$

need another input and another output

- decompose into multi-level logic (hopefully with CAD support)

- find common sub-expressions among functions

$$C0 = C3 + A' B X' + A D Y$$

$$C1 = Y + A' C5' + C' D' C6$$

$$C2 = C5 + A' B' D + A' C D$$

$$C3 = C4 + B D C5 + A' B' X'$$

$$C4 = D' Y + A' C D'$$

$$C5 = C' C4 + A Y + A' B X$$


$$C6 = A C4 + C C5 + C4' C5 + A' B' C$$

$$X = C' + D'$$

$$Y = B' C'$$

# Logical function unit

LFU  $\rightarrow$  ALU

 

- Multi-purpose function block
  - 3 control inputs to specify operation to perform on operands
  - 2 data inputs for operands
  - 1 output of the same bit-width as operands


C0	C1	C2	Function	Comments
0	0	0	1	always 1
0	0	1	$A + B$	logical OR
0	1	0	$(A \bullet B)'$	logical NAND
0	1	1	$A \text{ xor } B$	logical xor
1	0	0	$A \text{ xnor } B$	logical xnor
1	0	1	$A \bullet B$	logical AND
1	1	0	$(A + B)'$	logical NOR
1	1	1	0	always 0

3 control inputs: C0, C1, C2  
2 data inputs: A, B  
1 output: F

# Formalize the problem

C0	C1	C2	A	B	F
0	0	0	0	0	1
0	0	0	0	1	1
0	0	0	1	0	1
0	0	0	1	1	1
0	0	1	0	0	0
0	0	1	0	1	1
0	0	1	1	0	1
0	0	1	1	1	1
0	1	0	0	0	1
0	1	0	0	1	1
0	1	0	1	0	1
0	1	0	1	1	0
0	1	1	0	0	0
0	1	1	0	1	1
0	1	1	1	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	0	0	1	0
1	0	0	1	0	0
1	0	0	1	1	1
1	0	1	0	0	0
1	0	1	0	1	0
1	0	1	1	0	0
1	0	1	1	1	1
1	1	0	0	0	1
1	1	0	0	1	0
1	1	0	1	0	0
1	1	0	1	1	0
1	1	1	0	0	0
1	1	1	0	1	0
1	1	1	1	0	0
1	1	1	1	1	0

 choose implementation technology  
5-variable K-map to discrete gates  
multiplexor implementation




# Production line control

- Rods of varying length ( $\pm 10\%$ ) travel on conveyor belt
  - mechanical arm pushes rods within spec ( $\pm 5\%$ ) to one side
  - second arm pushes rods too long to other side
  - rods that are too short stay on belt
  - 3 light barriers (light source + photocell) as sensors
  - design combinational logic to activate the arms
- Understanding the problem
  - inputs are three sensors
  - outputs are two arm control signals
  - assume sensor reads "1" when tripped, "0" otherwise
  - call sensors A, B, C

# Sketch of problem
 
## ■ Position of sensors

- A to B distance = specification – 5%
- A to C distance = specification + 5%



# Formalize the problem

- Truth table
  - show don't cares

A	B	C	Function
0	0	0	do nothing
0	0	1	do nothing
0	1	0	do nothing
0	1	1	do nothing
1	0	0	too short
1	0	1	don't care
1	1	0	in spec
1	1	1	too long

logic implementation now straightforward  
just use three 3-input AND gates

"too short" =  $AB'C'$   
(only first sensor tripped)

"in spec" =  $A B C'$   
(first two sensors tripped)

"too long" =  $A B C$   
(all three sensors tripped)

# Calendar subsystem

- Determine number of days in a month (to control watch display)
  - used in controlling the display of a wrist-watch LCD screen
  - inputs: month, leap year flag
  - outputs: number of days
- Use software implementation to help understand the problem


```
integer number_of_days ( month, leap_year_flag) {  
    switch (month) {  
        case 1: return (31);  
        case 2: if (leap_year_flag == 1)  
                then return (29)  
                else return (28);  
        case 3: return (31);  
        case 4: return (30);  
        case 5: return (31);  
        case 6: return (30);  
        case 7: return (31);  
        case 8: return (31);  
        case 9: return (30);  
        case 10: return (31);  
        case 11: return (30);  
        case 12: return (31);  
        default: return (0);  
    }  
}
```

# Formalize the problem

## ■ Encoding:

- binary number for month: 4 bits
- 4 wires for 28, 29, 30, and 31  
one-hot – only one true at any time

## ■ Block diagram:

 

month	leap	28	29	30	31
0000	–	–	–	–	–
0001	–	0	0	0	1
0010	0	1	0	0	0
0010	1	0	1	0	0
0011	–	0	0	0	1
0100	–	0	0	1	0
0101	–	0	0	0	1
0110	–	0	0	1	0
0111	–	0	0	0	1
1000	–	0	0	0	1
1001	–	0	0	1	0
1010	–	0	0	0	1
1011	–	0	0	1	0
1100	–	0	0	0	1
1101	–	–	–	–	–
111–	–	–	–	–	–



# Choose implementation target and perform mapping

## ■ Discrete gates

□  $28 = m8' m4' m2 m1' \text{ leap}'$

□  $29 = m8' m4' m2 m1' \text{ leap}$

□  $30 = m8' m4 m1' + m8 m1$

□  $31 = m8' m1 + m8 m1'$

## ■ Can translate to S-o-P or P-o-S

month	leap	28	29	30	31
0000	—	—	—	—	—
0001	—	0	0	0	1
0010	0	1	0	0	0
0010	1	0	1	0	0
0011	—	0	0	0	1
0100	—	0	0	1	0
0101	—	0	0	0	1
0110	—	0	0	1	0
0111	—	0	0	0	1
1000	—	0	0	0	1
1001	—	0	0	1	0
1010	—	0	0	0	1
1011	—	0	0	1	0
1100	—	0	0	0	1
1101	—	—	—	—	—
111—	—	—	—	—	—

# Leap year flag

- Determine value of leap year flag given the year
  - For years after 1582 (Gregorian calendar reformation),
  - leap years are all the years divisible by 4,
  - except that years divisible by 100 are not leap years,
  - but years divisible by 400 are leap years.
- Encoding the year:
  - binary – easy for divisible by 4,  
but difficult for 100 and 400 (not powers of 2)
  - BCD – easy for 100,  
but more difficult for 4, what about 400?
- Parts:
  - construct a circuit that determines if the year is divisible by 4
  - construct a circuit that determines if the year is divisible by 100
  - construct a circuit that determines if the year is divisible by 400
  - combine the results of the previous three steps to yield the leap year flag

# Activity: divisible-by-4 circuit

BCD coded year

YM8 YM4 YM2 YM1 – YH8 YH4 YH2 YH1 – YT8 YT4 YT2 YT1 – YO8 YO4 YO2 YO1

- BCD coded year

YM8 YM4 YM2 YM1 – YH8 YH4 YH2 YH1 – YT8 YT4 YT2 YT1 – YO8 YO4 YO2 YO1

- Only need to look at low-order two digits of the year

all years ending in 00, 04, 08, 12, 16, 20, etc. are divisible by 4

- if tens digit is even, then divisible by 4 if ones digit is 0, 4, or 8
- if tens digit is odd, then divisible by 4 if the ones digit is 2 or 6

- Translates into the following Boolean expression

(where YT1 is the year's tens digit low-order bit,

YO8 is the high-order bit of year's ones digit, etc.) :

$$\begin{aligned} &YT1'(YO8'YO4'YO2'YO1' + YO8'YO4YO2'YO1' + YO8YO4'YO2'YO1') \\ &+ YT1(YO8'YO4'YO2YO1' + YO8'YO4YO2YO1') \end{aligned}$$

- Digits with values of 10 to 14 will never occur, simplify further to yield:

$$YT1'YO2'YO1' + YT1YO2YO1'$$

# Divisible-by-100 and divisible-by-400 circuits

- Divisible-by-100 just requires checking that all bits of two low-order digits are all 0:

$$YT8' YT4' YT2' YT1' \cdot YO8' YO4' YO2' YO1'$$

- Divisible-by-400 combines the divisible-by-4 (applied to the thousands and hundreds digits) and divisible-by-100 circuits

$$(YM1' YH2' YH1' + YM1 YH2 YH1')$$


$$\cdot (YT8' YT4' YT2' YT1' \cdot YO8' YO4' YO2' YO1' )$$

# Combining to determine leap year flag

- Label results of previous three circuits: D4, D100, and D400

$$\begin{aligned}\text{leap\_year\_flag} &= D4 (D100 \cdot D400')' \\ &= D4 \cdot D100' + D4 \cdot D400 \\ &= D4 \cdot D100' + D400\end{aligned}$$

# Implementation of leap year flag

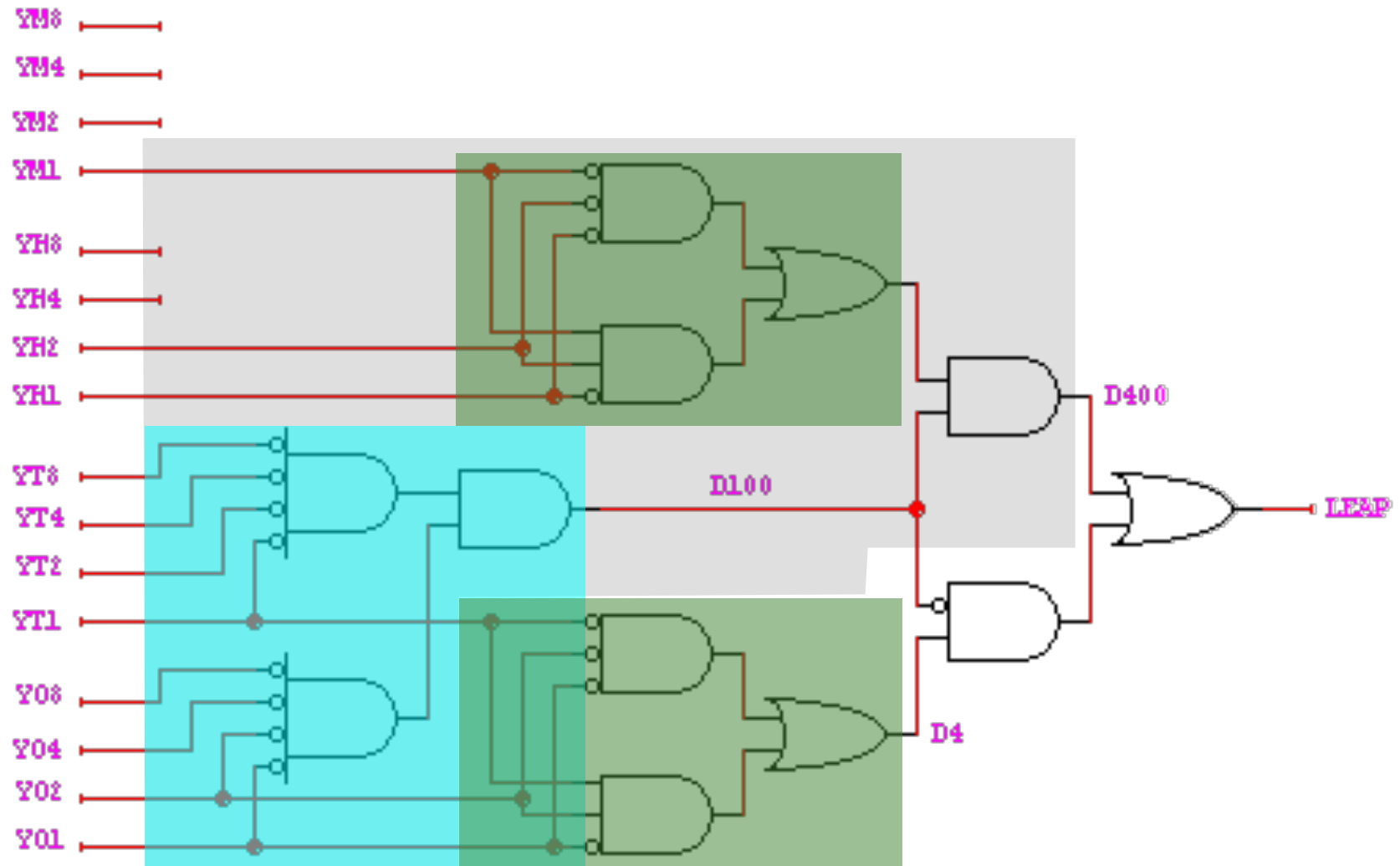

# Arithmetic circuits

- Excellent examples of combinational logic design
- Time vs. space trade-offs
  - doing things fast may require more logic and thus more space
  - example: carry lookahead logic
- Arithmetic and logic units
  - general-purpose building blocks
  - critical components of processor datapaths
  - used within most computer instructions

# Number systems

- Representation of positive numbers is the same in most systems
- Major differences are in how negative numbers are represented
- Representation of negative numbers come in three major schemes
  - sign and magnitude
  - 1s complement
  - 2s complement \*\*\*
- Assumptions
  - we'll assume a 4 bit machine word
  - 16 different values can be represented
  - roughly half are positive, half are negative




# Sign and magnitude

- One bit dedicate to sign (positive or negative)
  - sign: 0 = positive (or zero), 1 = negative
- Rest represent the absolute value or magnitude
  - three low order bits: 0 (000) thru 7 (111)
- Range for n bits
  - $\pm 2^{n-1} - 1$  (two representations for 0)
- Cumbersome addition/subtraction
  - must compare magnitudes to determine sign of result

$$0\ 100 = +4$$

$$1\ 100 = -4$$

 

# 1s complement

- If N is a positive number, then the negative of N (its 1s complement or  $N'$ ) is  $N' = (2^n - 1) - N$ 
  - example: 1s complement of 7

$$\begin{array}{rcl} 2^4 & = & 10000 \\ 1 & = & 00001 \\ \hline 2^4 - 1 & = & 1111 \\ 7 & = & 0111 \\ \hline & & 1000 = -7 \text{ in 1s complement form} \end{array}$$


- shortcut: simply compute bit-wise complement ( 0111  $\rightarrow$  1000 )

# 1s complement (cont'd)

- Subtraction implemented by 1s complement and then addition
- Two representations of 0
  - causes some complexities in addition
- High-order bit can act as sign bit

0 100 = + 4

1 011 = - 4

 


# 2s complement

- 1s complement with negative numbers shifted one position clockwise
  - ❑ only one representation for 0
  - ❑ one more negative number than positive numbers
  - ❑ high-order bit can act as sign bit

0 100 = + 4

1 100 = - 4

 

# 2s complement (cont'd)

- If N is a positive number, then the negative of N (its 2s complement or  $N^*$ ) is  $N^* = 2^n - N$

- example: 2s complement of 7

$$\begin{array}{rcl} & 2^4 & = 10000 \\ \text{subtract } 7 & = & \underline{0111} \\ & & 1001 = \text{repr. of } -7 \end{array}$$

- example: 2s complement of -7

$$\begin{array}{rcl} & 2^4 & = 10000 \\ \text{subtract } -7 & = & \underline{1001} \\ & & 0111 = \text{repr. of } 7 \end{array}$$

- shortcut: 2s complement = bit-wise complement + 1

- 0111  $\rightarrow$  1000 + 1  $\rightarrow$  1001 (representation of -7)
- 1001  $\rightarrow$  0110 + 1  $\rightarrow$  0111 (representation of 7)

# 2s complement addition and subtraction

- Simple addition and subtraction
  - simple scheme makes 2s complement the virtually unanimous choice for integer number systems in computers

$$\begin{array}{r} 4 \quad 0100 \\ + 3 \quad 0011 \\ \hline 7 \quad 0111 \end{array}$$

$$\begin{array}{r} -4 \quad 1100 \\ + (-3) \quad 1101 \\ \hline -7 \quad \cancel{1}1001 \end{array}$$

$$\begin{array}{r} 4 \quad 0100 \\ - 3 \quad 1101 \\ \hline 1 \quad \cancel{1}0001 \end{array}$$

$$\begin{array}{r} -4 \quad 1100 \\ + 3 \quad 0011 \\ \hline -1 \quad 1111 \end{array}$$

# Why can the carry-out be ignored?

- Can't ignore it completely
  - needed to check for **overflow** (see next two slides)
- When there is no overflow, carry-out may be true but can be ignored

–  $M + N$  when  $N > M$ : +

$$M^* + N = (2^n - M) + N = 2^n + (N - M)$$

ignoring carry-out is just like subtracting  $2^n$

–  $M + -N$  where  $N + M \leq 2^{n-1}$


$$(-M) + (-N) = M^* + N^* = (2^n - M) + (2^n - N) = 2^n - (M + N) + 2^n$$

ignoring the carry, it is just the 2s complement representation for  $-(M + N)$


# Overflow in 2s complement addition/subtraction
 
## ■ Overflow conditions

- add two positive numbers to get a negative number
- add two negative numbers to get a positive number



$$5 + 3 = -8$$

 

$$-7 - 2 = +7$$



# Overflow conditions

- Overflow when carry into sign bit position is not equal to carry-out

$$\begin{array}{r}
 5 \\
 - 3 \\
 \hline
 -8
 \end{array}$$

$$\begin{array}{r}
 \overset{\neq}{0}111 \\
 0101 \\
 \hline
 0011 \\
 1000
 \end{array}$$

overflow

$$\begin{array}{r}
 -7 \\
 - 2 \\
 \hline
 7
 \end{array}$$

$$\begin{array}{r}
 \overset{\neq}{1}000 \\
 1001 \\
 \hline
 1110 \\
 10111
 \end{array}$$

overflow

$$\begin{array}{r}
 5 \\
 + 2 \\
 \hline
 7
 \end{array}$$

$$\begin{array}{r}
 0000 \\
 0101 \\
 \hline
 0010 \\
 0111
 \end{array}$$

no overflow

$$\begin{array}{r}
 -3 \\
 - 5 \\
 \hline
 -8
 \end{array}$$

$$\begin{array}{r}
 1111 \\
 1101 \\
 \hline
 1011 \\
 11000
 \end{array}$$

no overflow

# Circuits for binary addition

- Half adder (add 2 1-bit numbers)
  - $\text{Sum} = A_i' B_i + A_i B_i' = A_i \text{ xor } B_i$
  - $\text{Cout} = A_i B_i$
- Full adder (carry-in to cascade for multi-bit adders)
  - $\text{Sum} = C_i \text{ xor } A \text{ xor } B$
  - $\text{Cout} = B C_i + A C_i + A B = C_i (A + B) + A B$


Ai	Bi	Sum	Cout
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Ai	Bi	Cin	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

# Full adder implementations

## ■ Standard approach


- 6 gates
- 2 XORs, 2 ANDs, 2 ORs

 
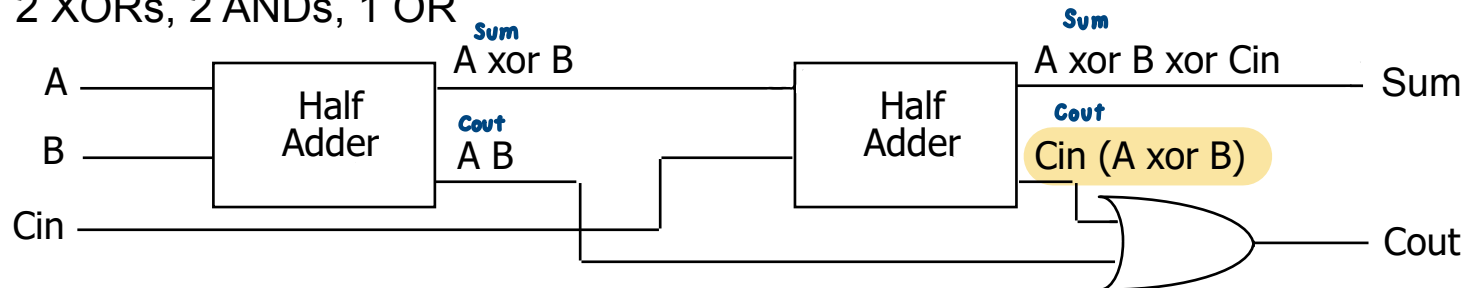
## ■ Alternative implementation

- 5 gates
- half adder is an XOR gate and AND gate
- 2 XORs, 2 ANDs, 1 OR

$$\text{Cout} = A B + \text{Cin} (A \text{ xor } B) = A B + B \text{Cin} + A \text{Cin}$$




# Adder/subtractor

Add' Subtract 0  $\Rightarrow S = A + B$

1  $\Rightarrow S = A - B$

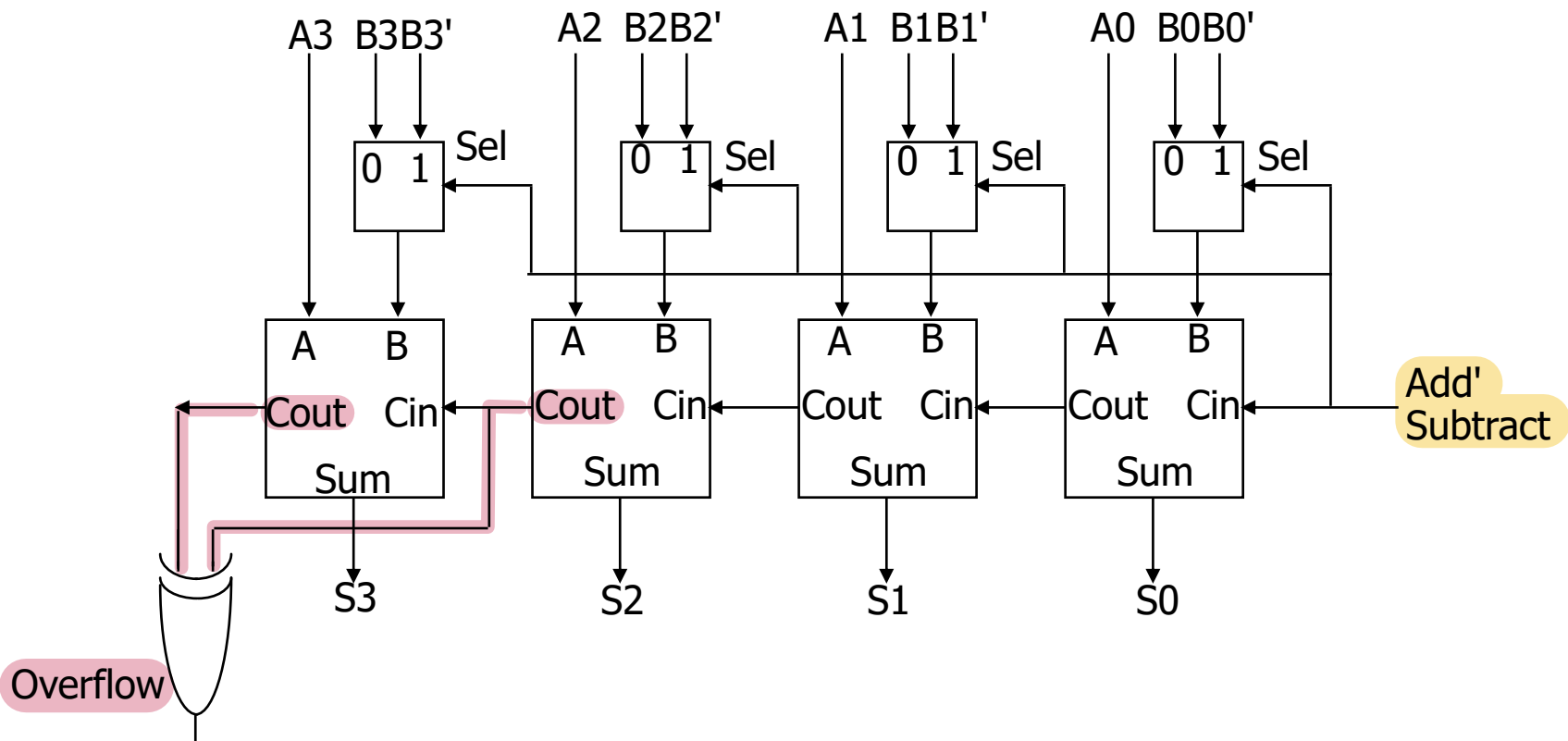- Use an adder to do subtraction thanks to 2s complement representation
  - $A - B = A + (-B) = A + B' + 1$
  - control signal selects B or 2s complement of B





# Ripple-carry adders

@ ← 1234

$\text{Max}(@_{\text{input}}) + 1$
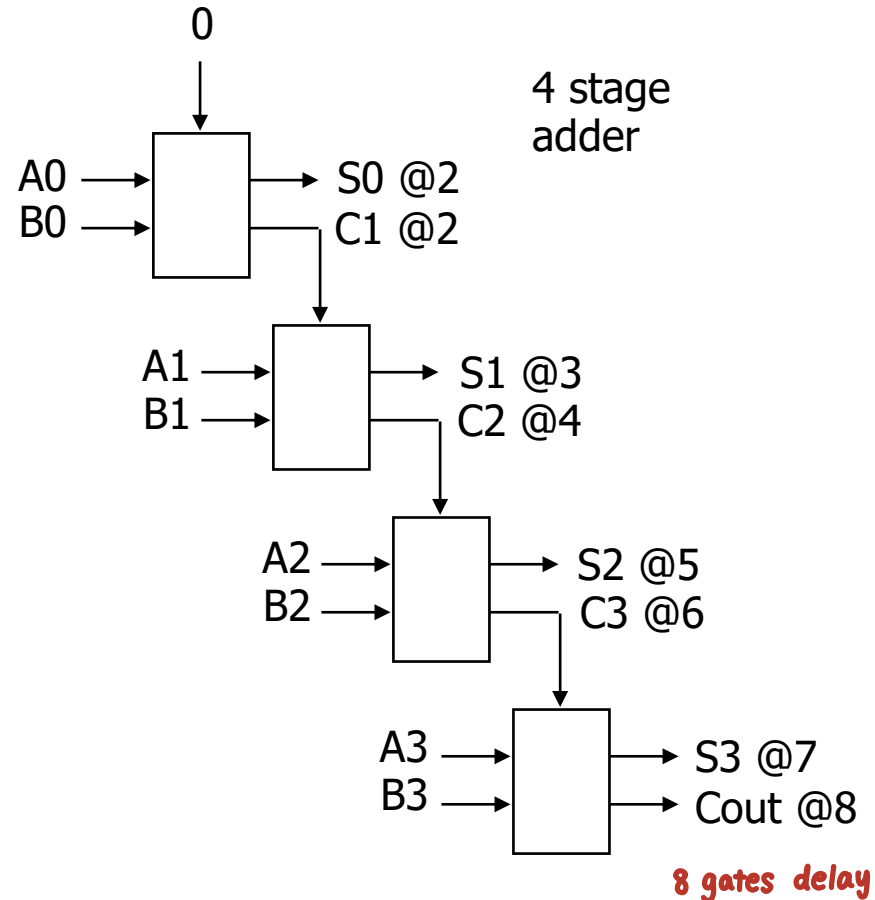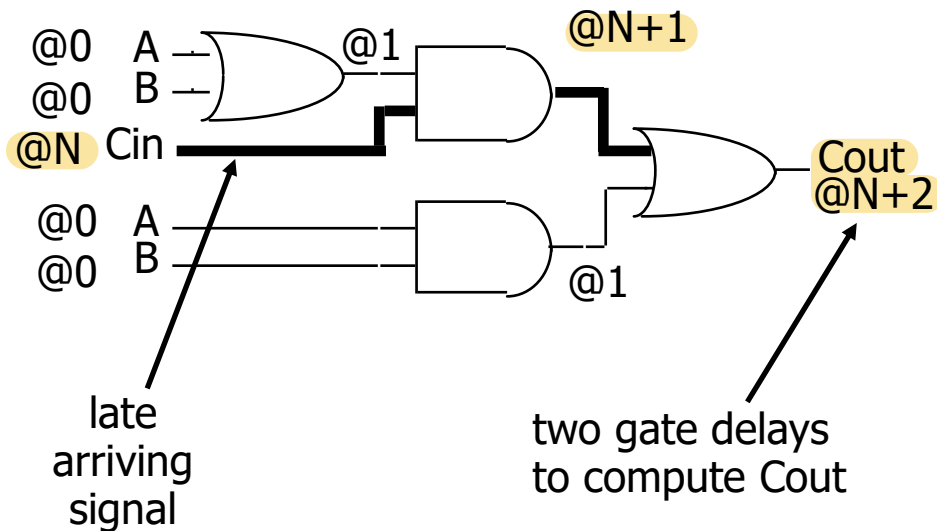
## ■ Critical delay

- the propagation of carry from low to high order stages




# Ripple-carry adders (cont'd)

$$\begin{array}{r} 1111 \\ 1111_2 \\ 0001 \\ \hline 10000 \end{array}$$
 
## ■ Critical delay

- the propagation of carry from low to high order stages
- $1111 + 0001$  is the **worst case** addition
- carry must **propagate** through all bits



# Carry-lookahead logic

## สร้างตัวแปรในมัลติเพล็กซ์

- Carry generate:  $G_i = A_i B_i$  \*
- must generate carry when  $A = B = 1$
- Carry propagate:  $P_i = A_i \oplus B_i$  \*
- carry-in will equal carry-out here
- Sum and Cout can be re-expressed in terms of generate/propagate:
  - $S_i = A_i \oplus B_i \oplus C_i$   
 $= P_i \oplus C_i$
  - $C_{i+1} = A_i B_i + A_i C_i + B_i C_i$   
 $= A_i B_i + C_i (A_i + B_i)$  🔍 *เท่ากันเฉพาะกรณีนี้!*  
 $= A_i B_i + C_i (A_i \oplus B_i)$   
 $= G_i + C_i P_i$

# Carry-lookahead logic (cont'd)

$$C_{i+1} = G_i + P_i C_i$$

- Re-express the carry logic as follows:

@3  $\square C_1 = G_0 + P_0 C_0 = G_1 + P_1 (G_0 + P_0 C_0)$

@3  $\square C_2 = G_1 + P_1 C_1 = G_1 + P_1 G_0 + P_1 P_0 C_0$

@3  $\square C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$

@3  $\square C_4 = G_3 + P_3 C_3 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0$





$\downarrow$   
 $G$ 
 $\downarrow$   
 $P$

- Each of the carry equations can be implemented with two-level logic
  - $\square$  all inputs are now directly derived from data inputs and not from intermediate carries
  - $\square$  this allows computation of all sum outputs to proceed in parallel




# Carry-lookahead implementation
    
## ■ Adder with propagate and generate outputs




 
increasingly complex logic for carries **แต่เร็ว**



# Carry-lookahead implementation (cont'd)
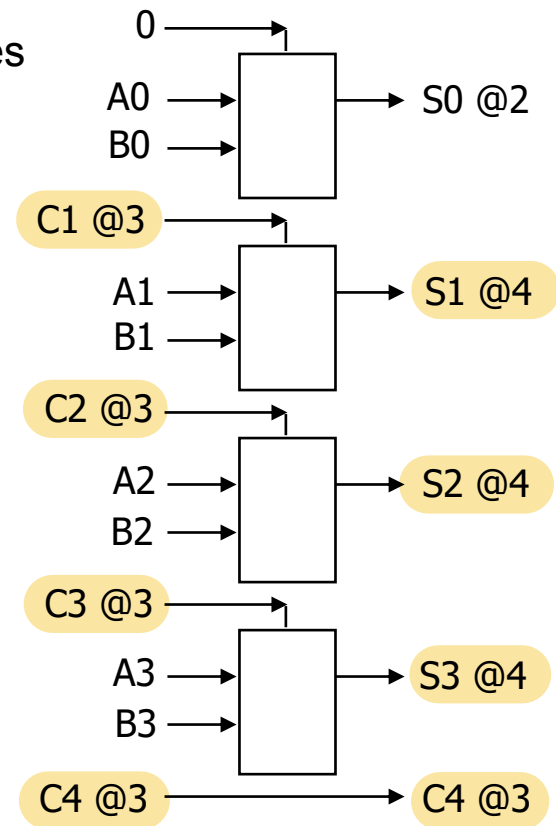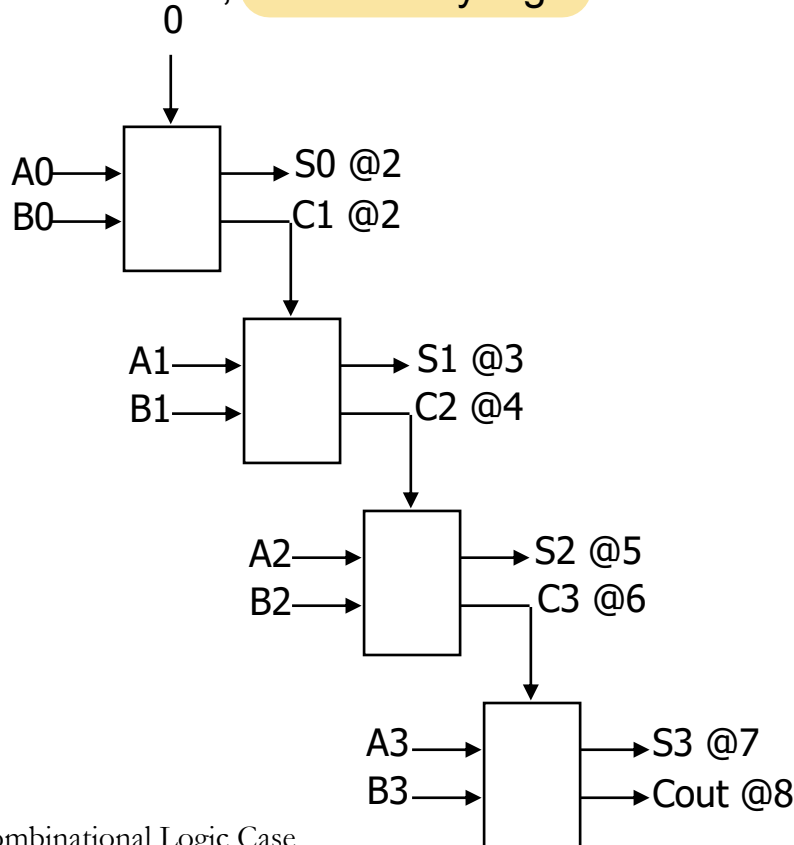
## LCU


- Carry-lookahead logic generates individual carries
  - sums computed much more quickly in parallel
  - however, cost of carry logic increases with more stages



# Carry-lookahead adder with cascaded carry-lookahead logic
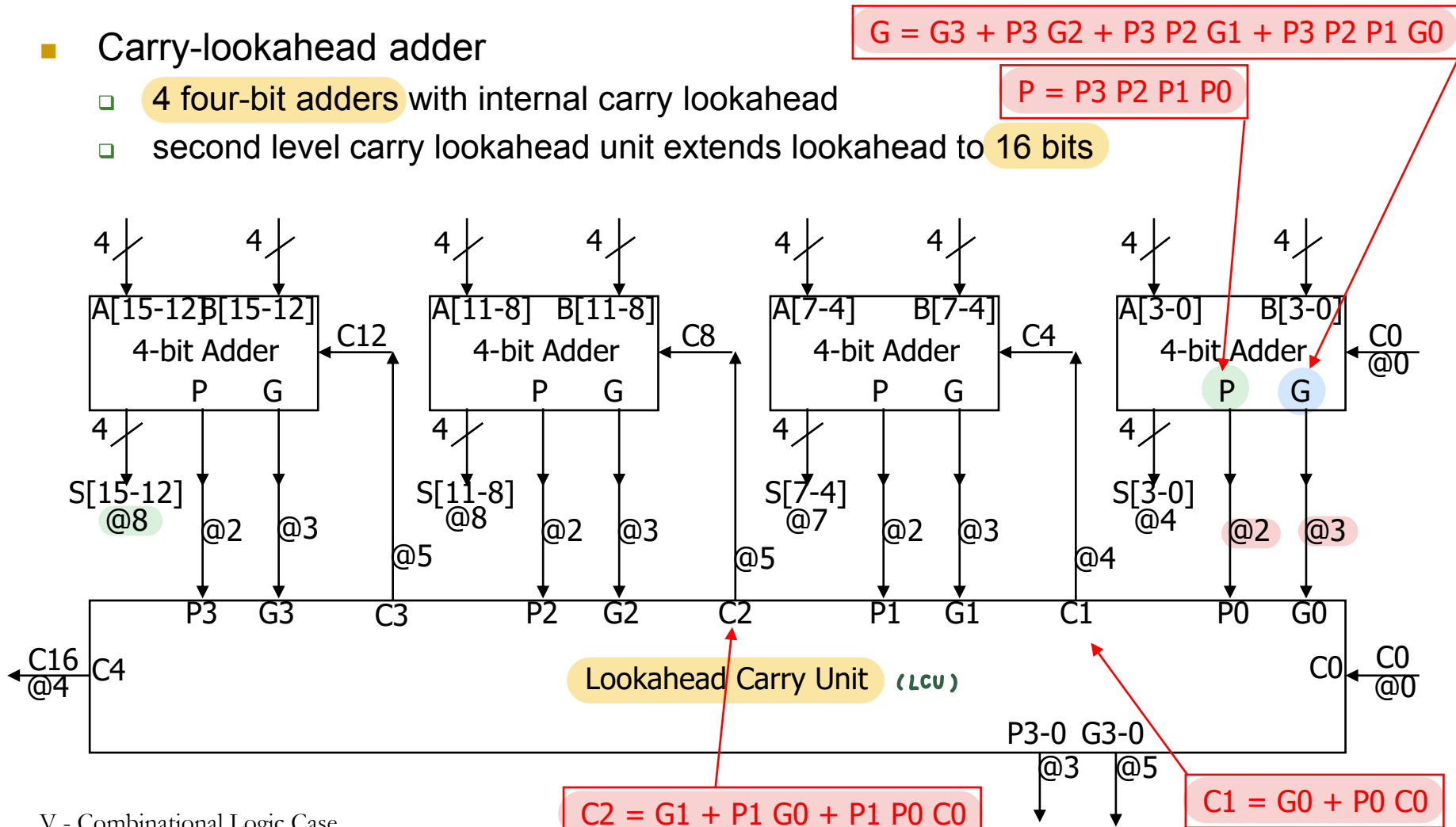
## ■ Carry-lookahead adder


- 4 four-bit adders with internal carry lookahead
- second level carry lookahead unit extends lookahead to 16 bits


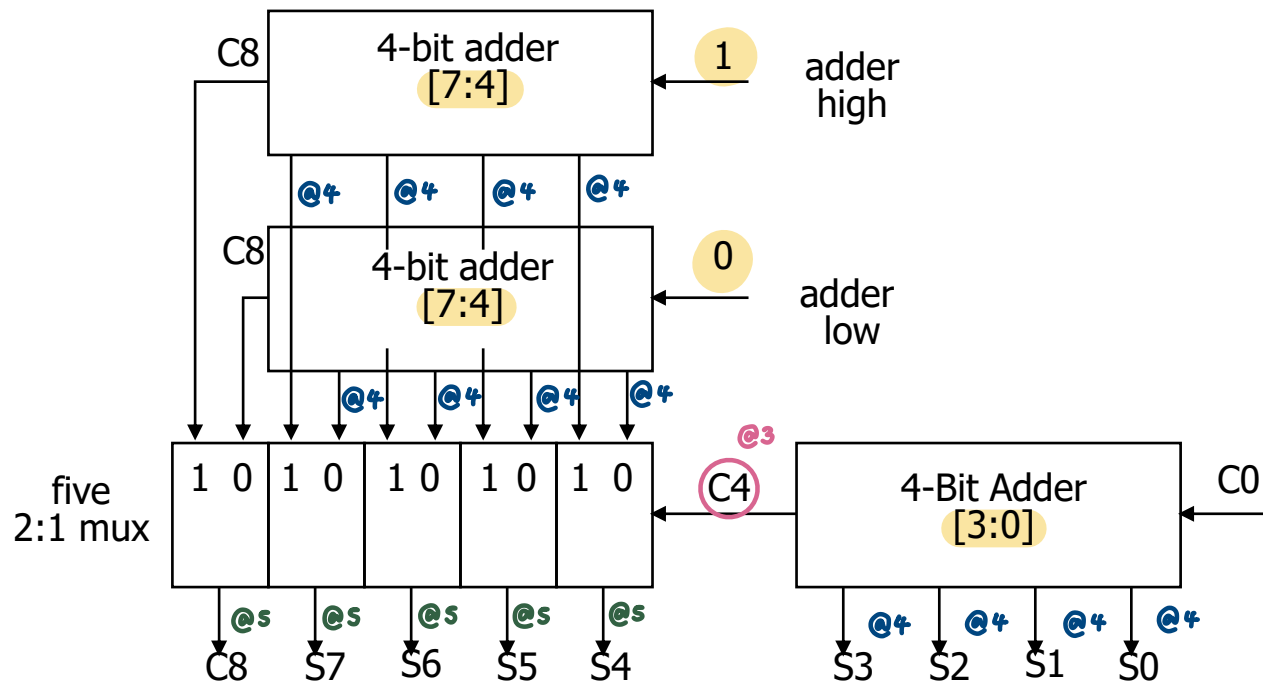
# Carry-select adder

*"8-bit"*

- Redundant hardware to make carry calculation go faster
  - compute two high-order sums in parallel while waiting for carry-in
  - one assuming carry-in is 0 and another assuming carry-in is 1
  - select correct result once carry-in is finally computed



# Arithmetic logic unit design specification

## **M = 0**, logical bitwise operations

S1	S0	Function	Comment
0	0	$F_i = A_i$	input $A_i$ transferred to output
0	1	$F_i = \text{not } A_i$	complement of $A_i$ transferred to output
1	0	$F_i = A_i \text{ xor } B_i$	compute XOR of $A_i, B_i$
1	1	$F_i = A_i \text{ xnor } B_i$	compute XNOR of $A_i, B_i$

## **M = 1**, **C0 = 0**, arithmetic operations

0	0	$F = A$	input A passed to output
0	1	$F = \text{not } A$	complement of A passed to output
1	0	$F = A \text{ plus } B$	sum of A and B
1	1	$F = (\text{not } A) \text{ plus } B$	sum of B and complement of A

## **M = 1**, **C0 = 1**, arithmetic operations

0	0	$F = A \text{ plus } 1$	increment A
0	1	$F = (\text{not } A) \text{ plus } 1$	twos complement of A
1	0	$F = A \text{ plus } B \text{ plus } 1$	increment sum of A and B
1	1	$F = (\text{not } A) \text{ plus } B \text{ plus } 1$	B minus A

logical and arithmetic operations  
not all operations appear useful, but "fall out" of internal logic


# Arithmetic logic unit design (cont'd)

## ■ Sample ALU – truth table

M	S1	S0	Ci	Ai	Bi	Fi	Ci+1
0	0	0	X	0	X	0	X
			X	1	X	1	X
	0	1	X	0	X	1	X
			X	1	X	0	X
	1	0	X	0	0	0	X
			X	0	1	1	X
			X	1	0	1	X
			X	1	1	0	X
	1	1	X	0	0	1	X
			X	0	1	0	X
1	0	0	X	1	0	0	X
			0	0	1	1	X
	0	1	0	0	1	1	X
			0	1	0	0	X
	1	0	0	0	0	0	0
			0	0	1	1	0
			0	1	0	1	0
			0	1	1	0	1
	1	1	0	0	0	1	0
			0	0	1	0	1
1	0	0	0	1	1	1	0
			1	1	X	0	1
	0	1	1	0	X	0	1
			1	1	X	1	0
	1	0	1	0	0	1	0
			1	0	1	0	1
			1	1	0	0	1
			1	1	1	1	1
	1	1	1	0	0	0	1
			1	0	1	1	1
			1	1	0	1	0
			1	1	1	0	1


# Arithmetic logic unit design (cont'd)
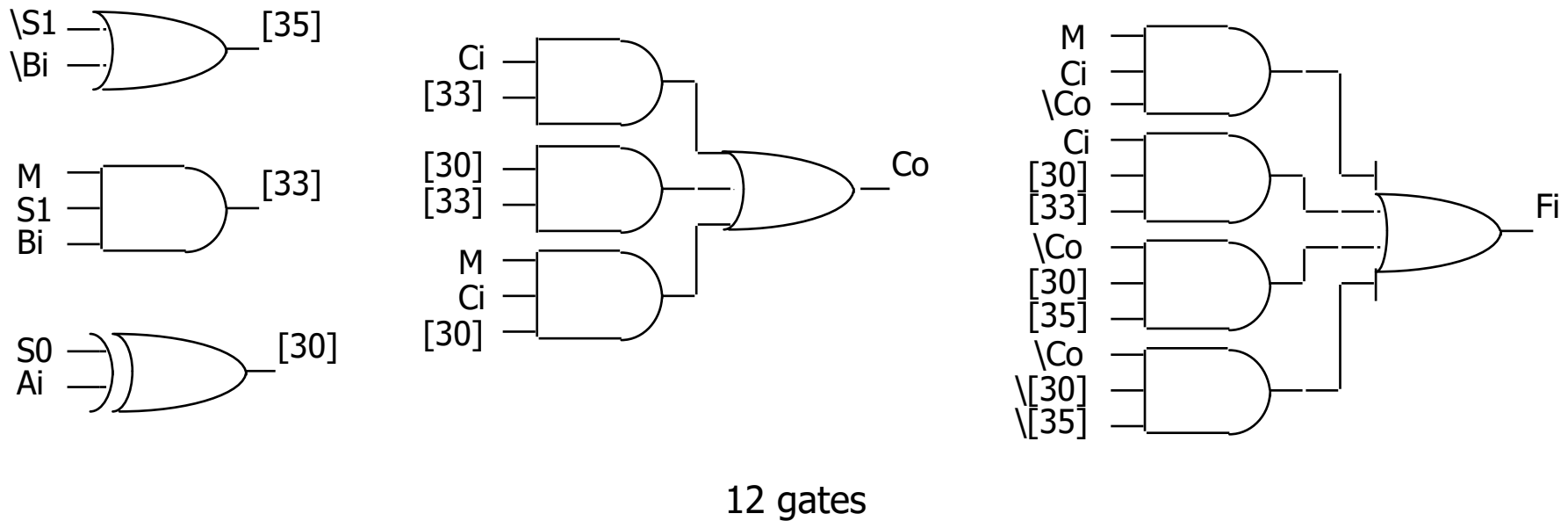
## ■ Sample ALU – multi-level discrete gate logic implementation



# Arithmetic logic unit design (cont'd)
 
## ■ Sample ALU – clever multi-level implementation



first-level gates

use S0 to complement Ai

S0 = 0 causes gate X1 to pass Ai

S0 = 1 causes gate X1 to pass Ai'

use S1 to block Bi

S1 = 0 causes gate A1 to make Bi go forward as 0  
(don't want Bi for operations with just A)

S1 = 1 causes gate A1 to pass Bi

use M to block Ci

M = 0 causes gate A2 to make Ci go forward as 0  
(don't want Ci for logical operations)

M = 1 causes gate A2 to pass Ci

other gates

for M=0 (logical operations, Ci is ignored)

$F_i = S1 \text{ Bi} \text{ xor } (S0 \text{ xor } Ai)$

$= S1'S0' (Ai) + S1'S0 (Ai') +$

$S1 S0' (Ai \text{ Bi}' + Ai' \text{ Bi}) + S1 S0 (Ai' \text{ Bi}' + Ai \text{ Bi})$

for M=1 (arithmetic operations)

$F_i = S1 \text{ Bi} \text{ xor } ((S0 \text{ xor } Ai) \text{ xor } Ci) =$

$Ci+1 = Ci (S0 \text{ xor } Ai) + S1 \text{ Bi} ((S0 \text{ xor } Ai) \text{ xor } Ci) =$

just a full adder with inputs S0 xor Ai, S1 Bi, and Ci



# Summary for examples of combinational logic

- Combinational logic design process
  - formalize problem: encodings, truth-table, equations
  - choose implementation technology (ROM, PAL, PLA, discrete gates)
  - implement by following the design procedure for that technology
- Binary number representation
  - positive numbers the same
  - difference is in how negative numbers are represented
  - 2s complement easiest to handle: one representation for zero, slightly complicated complementation, simple addition
- Circuits for binary addition
  - basic half-adder and full-adder
  - carry lookahead logic
  - carry-select
- ALU Design
  - specification, implementation